

2021 Digital IC Design

Homework 1: 4-bit Ripple Carry Adder

1. Introduction:

The ripple carry adder (RCA) circuit can be built using a cascade architecture of 1-bit full-adders. As a result, a 4-bit RCA comprises four 1-bit full-adders, which is shown in Fig. 1. In addition, a full-adder can also be constructed by two half-adders and one OR gate. Assume that x and y are 1-bit input signals and s and c are outputs standing for *sum* and *carry*. The computation of the half adder can be represented as equation (1). Fig. 2 illustrates the architecture of a half adder and a full adder. In this homework, please design a 4-bit ripple carry adder according to Fig. 1. You are suggested to design the circuit using hierarchy modules including series of half adders and full adders. The values are considered as unsigned integers.

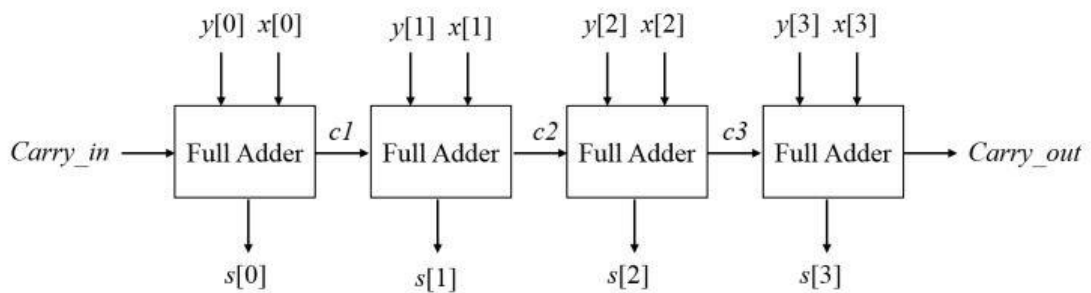


Fig. 1. The architecture of a 4-bit ripple carry adder.

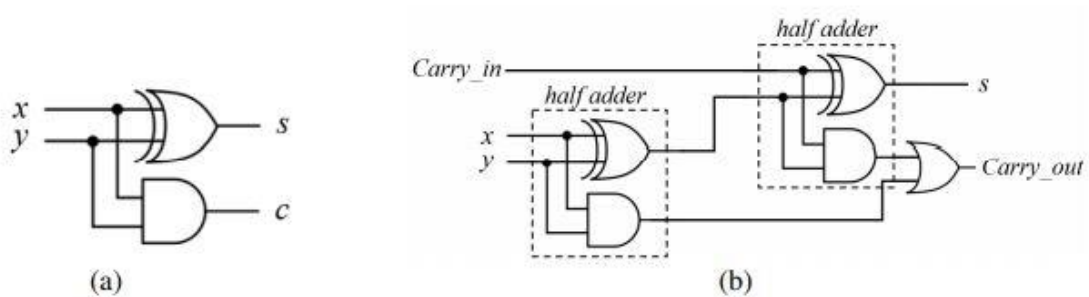


Fig. 2. The architecture of (a) an half-adder and (b) a full adder.

$$s = x \oplus y$$

(1)

$$c = x \cdot y$$

2. Design Specifications:

2.1 Block Overview

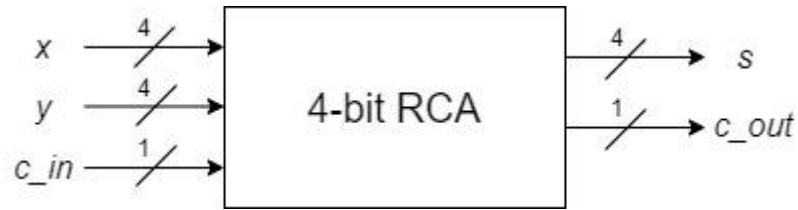


Fig. 3. The block overview.

2.2 I/O Interface

| Signal Name | I/O | width | Description |
|--------------|-----|-------|-------------|
| <i>x</i> | I | 4 | augend |
| <i>y</i> | I | 4 | summand |
| <i>c_in</i> | I | 1 | carry in |
| <i>s</i> | O | 4 | sum |
| <i>c_out</i> | O | 1 | carry out |

2.3 File Description

| File Name | Description |
|-----------|--|
| HA.v | The module of half-adder. |
| FA.v | The module of full adder. |
| RCA.v | The module of ripple carry adder, which is the top module in this design. |
| RCA_tb.v | The testbench file. The content in this file is not allowed to be modified. |

3. Scoring:

3.1 Functional Simulation [70%]

All of the result should be generated correctly, and you will get the following message in ModelSim simulation.

```
# 496 data is correct
# 497 data is correct
# 498 data is correct
# 499 data is correct
# 500 data is correct
# 501 data is correct
# 502 data is correct
# 503 data is correct
# 504 data is correct
# 505 data is correct
# 506 data is correct
# 507 data is correct
# 508 data is correct
# 509 data is correct
# 510 data is correct
# 511 data is correct
# -----PASS-----
# All data have been generated successfully!
```

Fig. 4. Functional simulation result.

3.2 Gate-Level Simulation [30%]

3.2.1 Synthesis

Your code should be synthesizable. After it is synthesized in Quartus, a file named *RCA.vo* will be obtained.

3.2.2 Simulation

All of the result should be generated correctly using *RCA.vo*, and you will get the following message in ModelSim simulation.

```
#      504 data is correct
#      505 data is correct
#      506 data is correct
#      507 data is correct
#      508 data is correct
#      509 data is correct
#      510 data is correct
#      511 data is correct
# -----PASS-----
# All data have been generated successfully!
```

Fig. 5. Gate-level simulation result.

Device : **Cyclone II EP2C70F896C8**

4. Submission:

4.1 Submitted files

You should classify your files into three directories and compress them to .zip format. The naming rule is HW1_studentID_name.zip. **If your file is not named according to the naming rule, you will lose five points.**

| | RTL category |
|-------|--|
| *.v | All of your Verilog RTL code |
| | Gate-Level category |
| *.vo | Gate-Level netlist generated by Quartus |
| *.sdo | Gate-Level netlist generated by Quartus |
| | Documentary category |
| *.pdf | The report file of your design (in pdf). |

4.2 Report file

Please follow the spec of report. You are asked to describe how the circuit is designed as detailed as possible, and the flow summary result is necessary in the report.

| Flow Summary | |
|------------------------------------|---|
| Flow Status | Successful - Mon Mar 22 14:57:10 2021 |
| Quartus II 64-Bit Version | 13.0.1 Build 232 06/12/2013 SP 1 SJ Web Edition |
| Revision Name | RCA |
| Top-level Entity Name | RCA |
| Family | Cyclone II |
| Device | EP2C70F896C8 |
| Timing Models | Final |
| Total logic elements | 10 / 68,416 (< 1 %) |
| Total combinational functions | 10 / 68,416 (< 1 %) |
| Dedicated logic registers | 0 / 68,416 (0 %) |
| Total registers | 0 |
| Total pins | 14 / 622 (2 %) |
| Total virtual pins | 0 |
| Total memory bits | 0 / 1,152,000 (0 %) |
| Embedded Multiplier 9-bit elements | 0 / 300 (0 %) |
| Total PLLs | 0 / 4 (0 %) |

Fig. 6. The flow summary.

4.3 Note

Please submit your .zip file to folder HW1 in moodle.

Deadline: 2021/4/12 23:55

If you have any problem, please contact TA by email

qweszxc12345@gmail.com

lt2es.93039@gmail.com